






# Ohm Comforts



## TESTING YOUR METER SKILLS

COLLECT A QUIZ BOARD & PEN  
OK Students lets see how much you know.

1) Name that meter

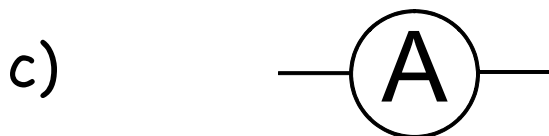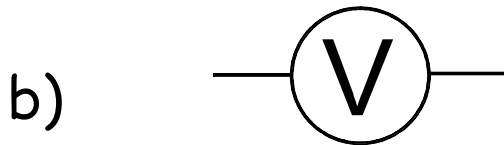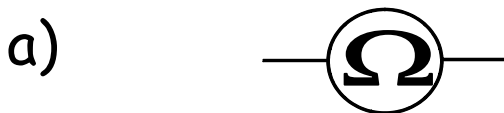

2) Which terminal is always used on a meter?

3) Which meter mustn't be plugged in with a power supply?

4) Which meter goes in parallel?


5) Which meter goes in series?




# Ohm Comforts



6) Name meter X

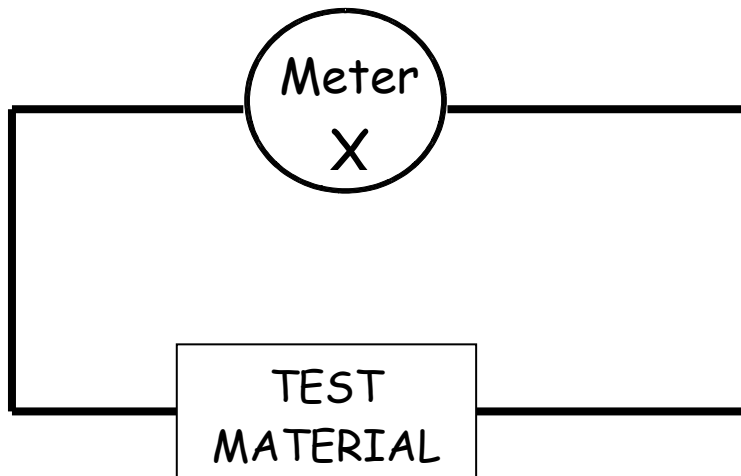

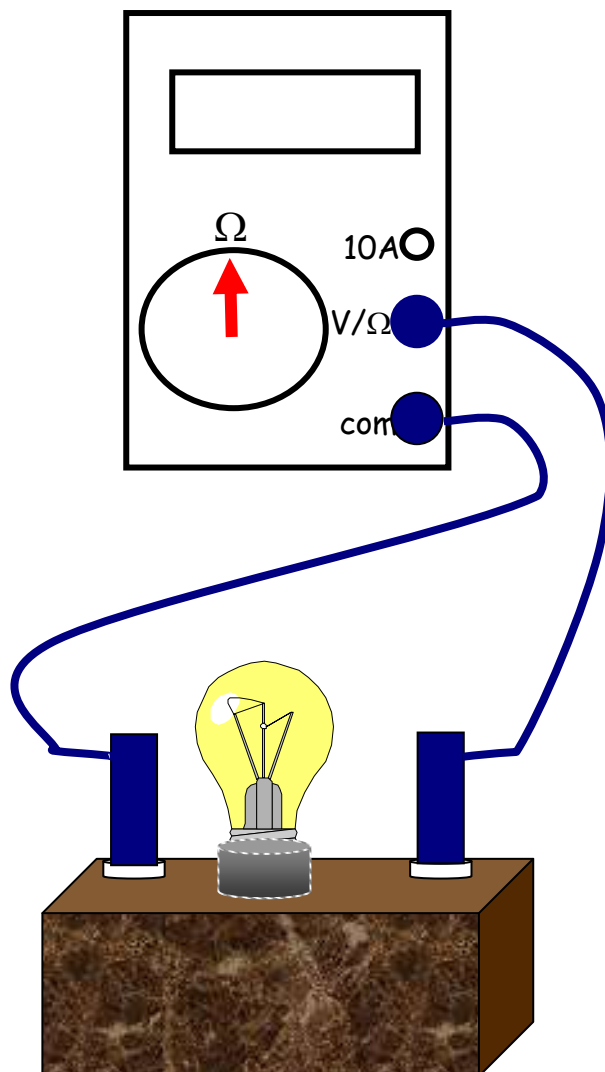7) What is this circuit being used to find?






# Ohm Comforts



8) Name meter Y

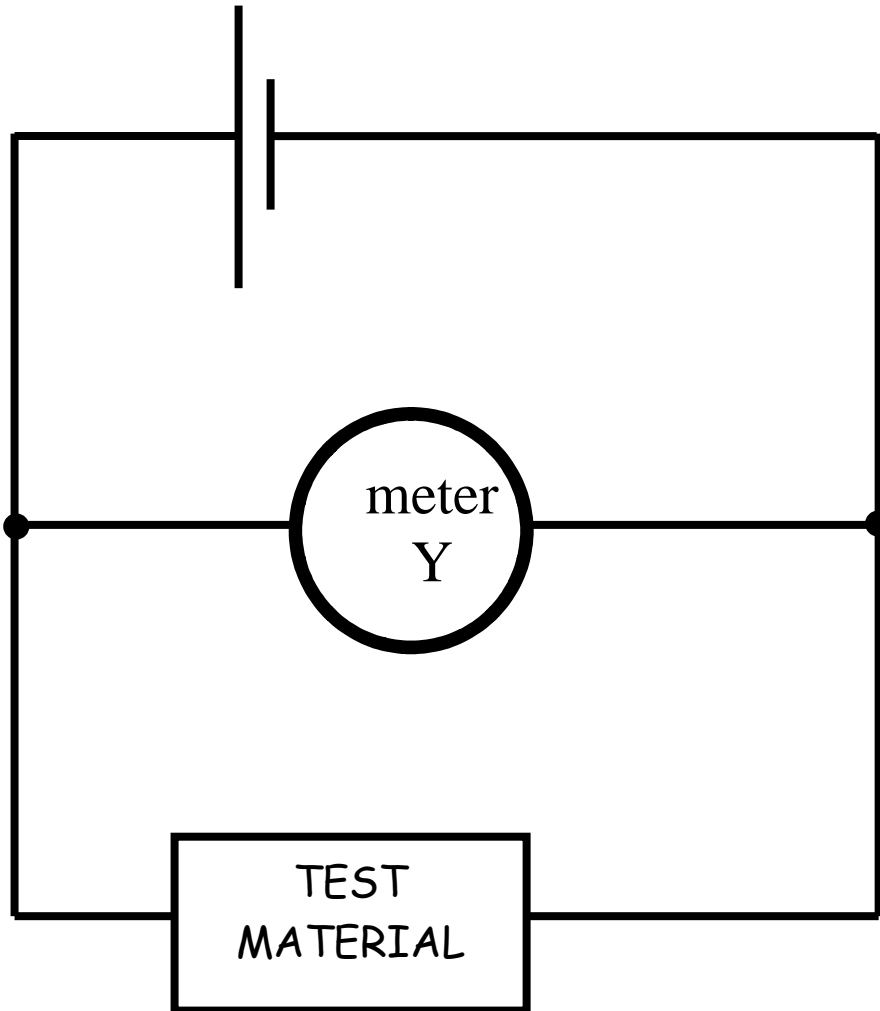



# Ohm Comforts



## TASK

Each group needs to complete at least 2 of the following tasks

1. Measure the current at 5 places in a series circuit containing 2 cells, 3 bulbs and a switch Draw the circuit diagram and record your findings.
2. Measure the current at 5 places in a parallel circuit containing 2 cells, 3 bulbs and a switch Draw the circuit diagram and record your findings.
3. Measure how the resistance changes with the length of a wire. Record your findings
4. Measure the voltage across 5 places in a series circuit containing 2 cells, 3 bulbs and a switch Draw the circuit diagram and record your findings.
5. Measure the voltage across 5 places in a parallel circuit containing 2 cells, 3 bulbs and a switch Draw the circuit diagram and record your findings.



# Ohm Comforts



6. (Extension Measure the how the resistance changes when light bulbs are added in series and parallel)


## HELPFUL HINTS

length (cm)	Resistance ( $\Omega$ )
10	
20	
30	
40	
50	





# Ohm Comforts

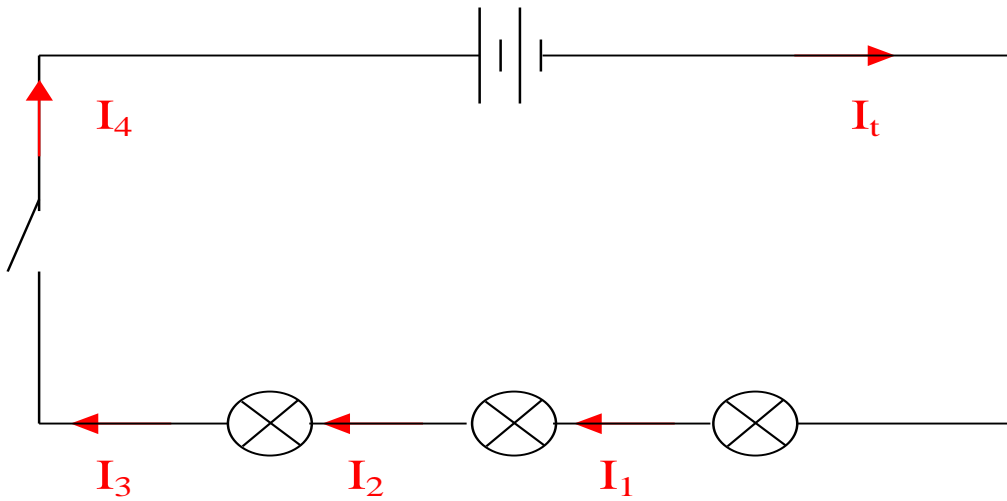


Position	Current (A)
$I_t$	
$I_1$	
$I_2$	
$I_3$	
$I_4$	




# Ohm Comforts



Position	Current (A)
$I_t$	
$I_1$	
$I_2$	
$I_3$	
$I_4 (I_1+I_2)$	
$I_5$	

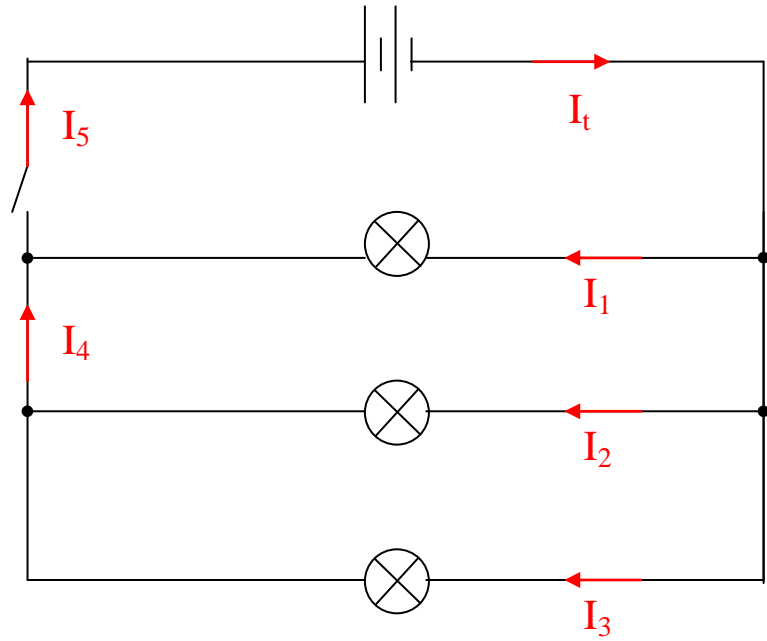

Position	VOLTAGE (V)
$V_s$	
$V_1$	
$V_2$	
$V_3$	

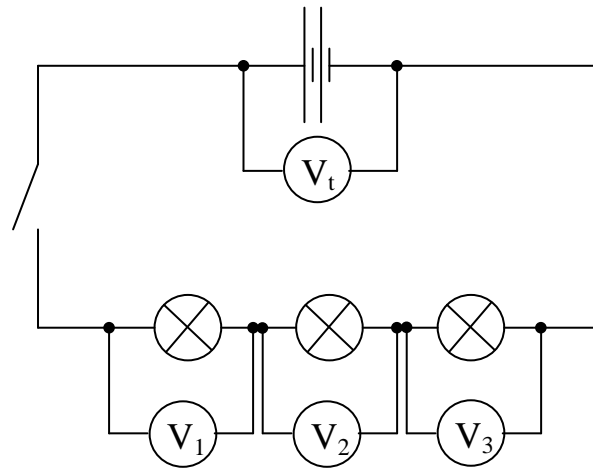



# Ohm Comforts



Position	VOLTAGE (V)
$V_s$	
$V_1$	
$V_2$	
$V_3$	

