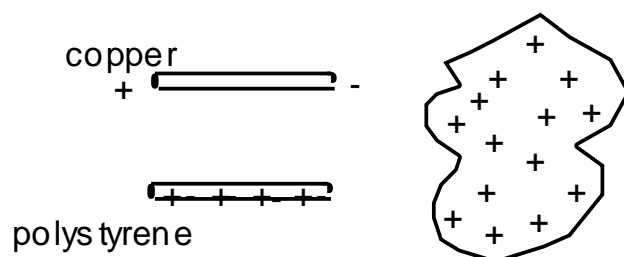


ELECTRIC FIELDS & RESISTORS IN CIRCUITS/ TUTORIAL ANSWERS

ANSWERS FOR TUTORIAL 1

1.



2. $\mathbf{X} = 15^\circ$ since the field is uniform.

3. The electric force on the drop is given by

$$\begin{aligned} F_e &= Q \times E \\ &= 3 \times 10^{-12} \times 4 \times 10^4 \\ &= 1.2 \times 10^{-7} \end{aligned}$$

Since the drop is *floating*, the electric force, $1.2 \times 10^{-7} \text{N}$, is the same as its weight.

4. The electrical work done is given by $W = QV$

$$\begin{aligned} &= 5 \times 10^{-12} \text{ H} (150 - 10) \\ &= 7 \times 10^{-10} \end{aligned}$$

Since the motion is caused by the sphere's weight, the work done by the gravitational field is $7 \times 10^{-10} \text{J}$.

ANSWERS FOR TUTORIAL 2

1. a) $P=VI$ gives $48=12 \times I$
Thus $I = 4$
The current in the lamp is 4A

b)

$$\frac{V}{I} = R \Rightarrow \frac{12}{4} = R$$
$$\Rightarrow R = 3$$

The lamp's resistance is 3Ω

2. $\frac{9.6}{I} = 2000 \Rightarrow I = 4.8 \times 10^{-3}$

The current in the resistor is 4.8mA

3.

$$R = 3 \times 125 \times 10^{-3}$$
$$= 375 \times 10^{-3}$$

$$\frac{V}{4} = 375 \times 10^{-3} \Rightarrow V = 1.5$$

The wire has a p.d. of 1.5V across it.

ANSWERS FOR TUTORIAL 3

1. a)

$$W = QV \quad \Rightarrow \quad W = 15 \times 1200 = 1.8 \times 10^4$$

There are 18000J of work done.

$$b) \quad P = \frac{W}{t} \Rightarrow \quad P = \frac{1.8 \times 10^4}{600} \\ = 30$$

It is a 30W device.

$$c) \quad I = \frac{Q}{t} \Rightarrow \quad I = \frac{15}{600} \\ = 2.5 \times 10^{-2}$$

The current in the device is 25mA

d)

$$V \times I = \frac{\text{joules}}{\text{coulombs}} \times \frac{\text{coulombs}}{\text{sec}} \\ = \frac{\text{joules}}{\text{sec}}$$

The product of *volts* and *amps* is *watts*.

2.

$$P = VI \Rightarrow \quad 24 = 12 \times I \\ \Rightarrow \quad I = 2$$

$$\frac{V}{I} = R \quad \Rightarrow \quad \frac{12}{2} = R \\ \Rightarrow \quad R = 6$$

The bulb has a resistance of 6Ω

$$E = V + Ir \quad \Rightarrow \quad 12 = 9 + 3 \times r$$

$$3. \quad \Rightarrow \quad r = 1$$

The battery's internal resistance is 1Ω

$$4. \quad a) \quad E = IR + Ir$$

A 'short circuit' means that $R = \text{zero}$

Thus the equation above gives $12 = 0 + I \times 0.001$ or $I = 1.2 \times 10^4$

The short circuit current is $12000A$

$$b) \quad 1.5 = 0 + I \times 1.25$$

Thus $I = 1.2$

The short circuit current of a dry cell is $1.2A$

5.

$$E = V + Ir \quad \Rightarrow \quad E = 5.7 + 1.5 \times r \text{ ----- (1)}$$

$$\text{and} \quad E = 4.6 + 2 \times r \text{ ----- (2)}$$

$$\text{Subtract :} \quad \Rightarrow \quad 0 = 1.1 - 0.5 \times r$$

$$\Rightarrow \quad r = 2.2$$

Substitute this value of r in equation (1) to get

$$E = 5.7 + 1.5 \times 2.2$$

$$= 5.7 + 3.3$$

$$= 9$$

The e.m.f. of the power supply is **9V** and its internal resistance is **2.2Ω**.

ANSWERS FOR TUTORIAL 4

$$1. \quad R = R_1 + R_2 + R_3 \Rightarrow R = 10 + 200 + 1000 \\ \Rightarrow R = 1210$$

The total resistance is 1210Ω

$$2. \quad R = R_1 + R_2 + R_3 \Rightarrow 250 = 95 + R + 115 \\ \Rightarrow R = 40$$

The unknown resistance is 40Ω

$$3. \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow \frac{1}{R} = \frac{3}{900} \\ \Rightarrow R = \frac{900}{3} \\ = 300$$

The equivalent resistance is 300Ω

$$4. \quad \frac{1}{250} = \frac{1}{500} + \frac{1}{R} \Rightarrow \frac{1}{R} = \frac{1}{250} - \frac{1}{500} = \frac{1}{500} \\ \Rightarrow R = 500$$

The unknown resistance is 500Ω

$$5. \quad \frac{1}{R} = \frac{1}{200} + \frac{1}{300} + \frac{1}{600} = \frac{3+2+1}{600} = \frac{6}{600} \\ \Rightarrow R = \frac{600}{6} = 100$$

The equivalent resistance is 100Ω

6.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \Rightarrow \quad \frac{1}{R} = \frac{4}{4}$$

$$\Rightarrow R = \frac{4}{4}$$
$$= 1$$

The equivalent resistance is 1Ω

7.

$$\frac{1}{18.75} = \frac{1}{75} + \frac{1}{R} \quad \Rightarrow \quad \frac{1}{R} = \frac{1}{18.75} - \frac{1}{75} = \frac{1}{25}$$

$$\Rightarrow R = 25$$

The unknown resistance is 25Ω

ANSWERS FOR TUTORIAL 5

1.

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow \frac{126}{147} = \frac{228}{R}$$

$$\Rightarrow \frac{147}{126} = \frac{R}{228}$$

$$\Rightarrow R = 266$$

The unknown resistance is 266Ω

2.

$$\frac{350}{1050} = \frac{R}{450} \Rightarrow R = 150$$

R has a value of 150Ω

3. Yes; the resistors do not have the same ratio in each branch and so the micro-ammeter registers a current which requires a p.d. across it. If you care to calculate the actual values, you find that **A** is at 8V and **B** at 6V. This gives a 2V p.d. between **B** and **A**.

ANSWERS FOR TUTORIAL 6

$$1. \quad a) \quad R = R_1 + R_2 + R_3 \Rightarrow R = 2 + 4 + 6$$

$$\Rightarrow R = 12$$

The total resistance for this circuit is 12Ω .

$$b) \quad \text{Ohm's law gives } I = \frac{24}{12} = 2$$

The current is 2A

c) Apply Ohm's law to each resistor in turn to get:
 $V_2 = 2 \times 2 = 4$; $V_4 = 2 \times 4 = 8$; $V_6 = 2 \times 6 = 12$
 The p.d.'s are 4V, 8V and 12V across the 2, 4 and 6 Ω resistors respectively.

$$2. \quad a) \quad \frac{1}{R} = \frac{1}{2} + \frac{1}{4} + \frac{1}{6} = 0.5 + 0.25 + 0.167 = 0.917$$

$$\Rightarrow R = \frac{1}{0.917} = 1.09$$

The total is 1.09Ω

N.B. When there are several resistors in parallel, their equivalent resistance is *always* a little less than the least resistance in use.

$$b) \quad \text{Apply Ohm's law to each resistor in turn.}$$

$$I_2 = \frac{12}{2} = 6; \quad I_4 = \frac{12}{4} = 3; \quad I_6 = \frac{12}{6} = 2$$

The currents are 6A, 3A and 2A in the 2, 4 and 6 Ω resistors respectively.

3. a) The reading increases since the 1000 Ω resistor which limits the ammeter current to 10 μ A has been removed.
- b) It doubles the current in each branch of the network which still leaves the micro-ammeter reading zero.

4. Since the out-of-balance current and resistance are directly proportional,

$$\frac{I_1}{R_1} = \frac{I_2}{R_2} \quad \Rightarrow \quad \frac{30 \times 10^{-6}}{25} = \frac{36 \times 10^{-6}}{R_2}$$
$$\Rightarrow \quad R_2 = 30$$

The resistance is 30Ω.

5. The strain gauge is made into one arm of a Wheatstone bridge which is then balanced with another identical strain gauge in an unstrained position. This means that any future strain on the working gauge causes an out-of-balance resistance whose size can be measured from the size of the out-of-balance current. We then apply different weights to the hacksaw blade and use the out-of-balance current as a measure of the amount of bending.