

Describe a.c and
d.c.

Peak Voltage & Peak
current

1

2

V_{rms}

Formulae for

V_{rms} & I_{rms}

I_{rms}

3

4

Find frequency of
an a.c. supply from
an oscilloscope

Find the peak
voltage from an
oscilloscope

5

6

Use appropriate
relationships to solve
problems involving
potential difference,
current, power and
resistance

Use appropriate
relationships to solve
problems involving
potential divider
circuits.

7

8

Define
electromotive force
(EMF)

Internal resistance

9

10

The maximum voltage / current produced by an a.c. supply. These can be measured using an oscilloscope.

a.c. is a current which changes direction and instantaneous value with time.

d.c. is a current which travels in one direction.

$$V_{rms} = \frac{V_{peak}}{\sqrt{2}}$$

$$I_{rms} = \frac{I_{peak}}{\sqrt{2}}$$

The values given to an a.c supply that would have the same heating effect as an equivalent d.c supply

Count the number of divisions for the amplitude of the wave. Multiply this by the number of volts per division.

Find the period (time for one wave (T)).

$$\text{frequency} = \frac{1}{T}$$

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_s$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$V = IR$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

$$R_T = R_1 + R_2 + \dots$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

The resistance of a power supply.

The total amount of energy given to each coulomb of charge by a power supply.

Lost volts

Terminal
potential
difference

11

12

Short circuit
current

$$E = V_{\text{tpd}} + Ir$$

13

14

Describe an
experiment to find
the EMF and internal
resistance of a supply.

Be able to find the
EMF, internal
resistance and short
circuit current from a
graph of V_{tpd} vs
current

15

16

Define
Capacitance

$$C = \frac{Q}{V}$$

17

18

$$Q = It$$

Find the total energy
stored in a capacitor
from a charge vs
potential difference
graph.

19

20

$$V_{\text{tpd}} = E - V_{\text{lost}}$$

The voltage across the terminals of a supply when a load resistance is connected.

$$V_{\text{lost}} = Ir$$

The voltage across the internal resistance when a load resistance is connected.

$$E = V_{\text{tpd}} + V_{\text{lost}}$$

$$E = IR + Ir$$

$$E = I(R + r)$$

The current drawn from a supply when the terminals are connected together with no load resistance. This can produce a large current and can be dangerous.

$$I = E/r$$


$$V = -rI + E$$

$$(Y = mx + c)$$

EMF = Y-intercept

Internal resistance = negative the gradient.

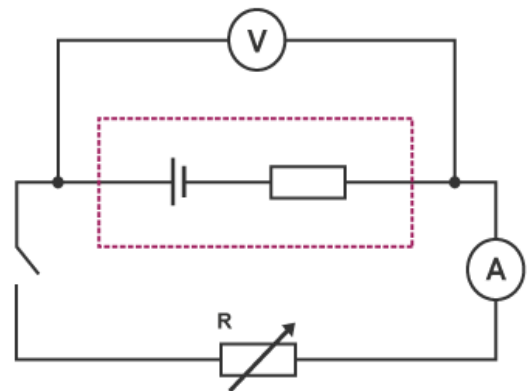Short circuit current = current when $V_{\text{tpd}} = 0$



C = Capacitance - measured in farads (F)

Q = Charge - measured in coulombs (C)

V = potential difference - measured in volts (V)

A capacitor of 1 farad capacitance will store 1 coulomb of charge when the potential difference across it is 1 volt.

The energy stored by a capacitor is equal to the area under a charge vs potential difference graph.

Q = Charge - measured in coulombs (C)

I = Current - measured in amperes (A)

t = time - measured in seconds (s)

Equations to find the energy stored by a capacitor

21

Sketch a graph of voltage vs time for a charging capacitor

22

Sketch a graph of current vs time for a charging capacitor

23

Sketch a graph of voltage vs time for a discharging capacitor

24

Sketch a graph of current vs time for a discharging capacitor

Describe the effect of changing resistance on the charging and discharging curves for a capacitor?

25

26

Describe the effect of changing capacitance on the charging and discharging curves for capacitors?

Describe experiments to measure the current and voltage for charging and discharging capacitors

27


28

Conduction band







Valence band

29

30

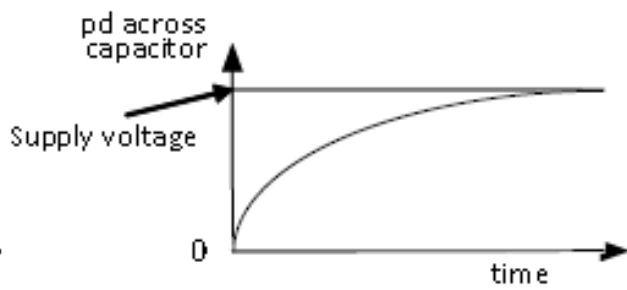
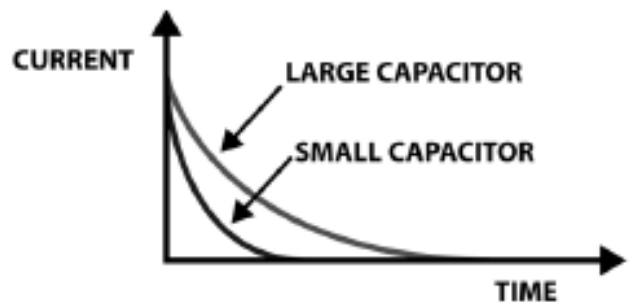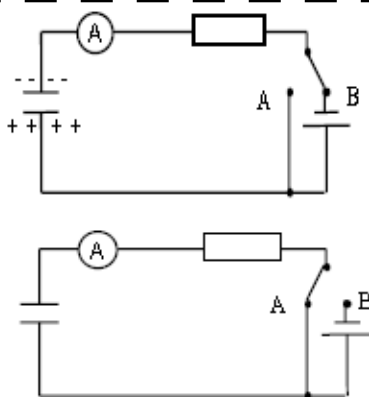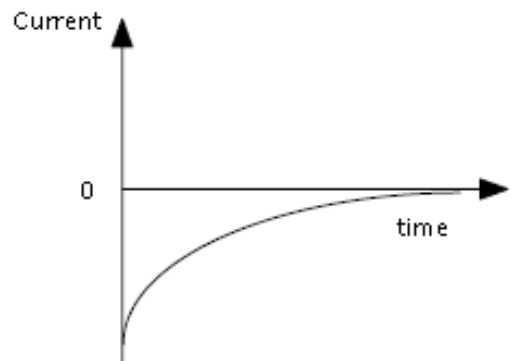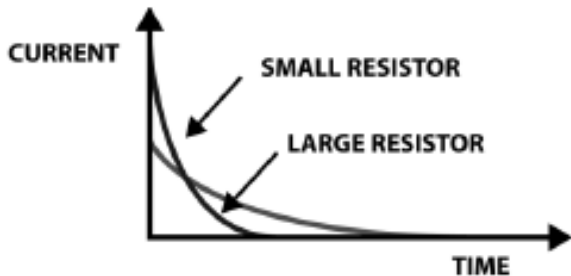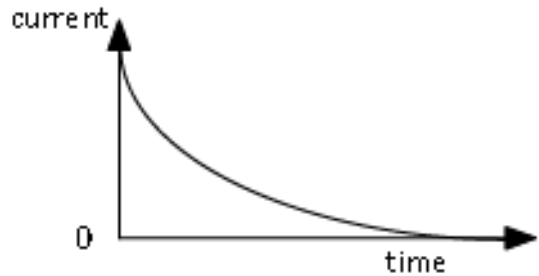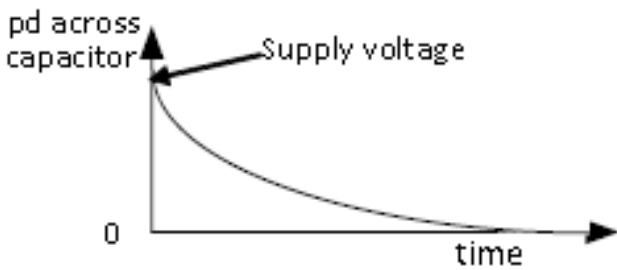
$$E = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$



The range of possible energies an electron can have and still be part of an atom.

The range of possible energy levels for free electrons. These are electrons that have gained enough energy to escape the valence band.

Describe the band structure of insulators, semiconductors and conductors

31

Describe how an n-type semiconductor is formed

32

Describe how a p-type semiconductor is formed

33

P-n junction

34

Forward bias

Reverse bias

35

36

Describe how an LED emits light

Photovoltaic mode (solar cells)

37



38

Photoconductive mode (LDR)




39

40

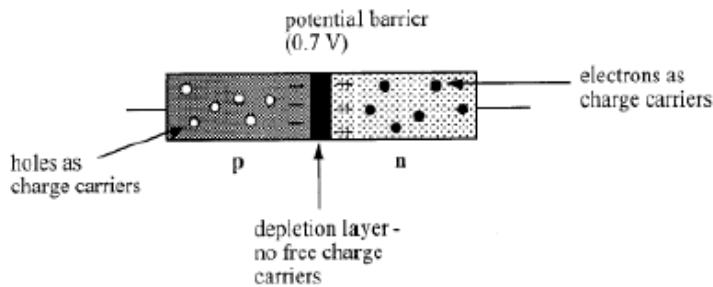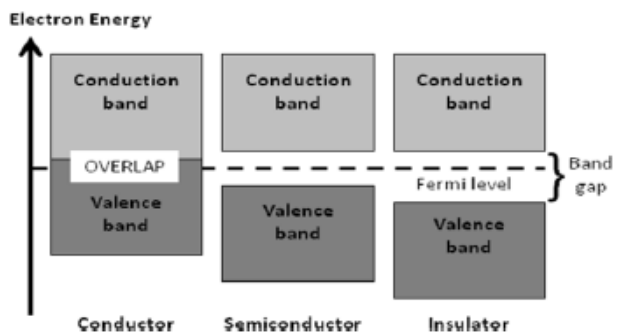
A material such as silicon has impurities added with an extra outer electron e.g. Arsenic



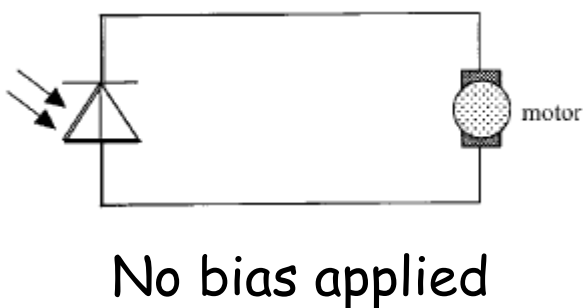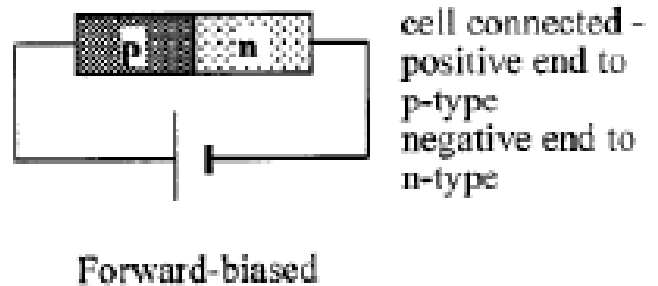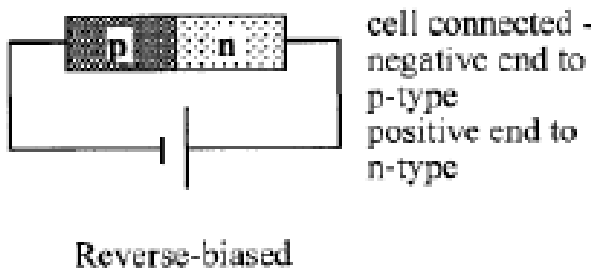A material such as silicon has impurities added with one fewer extra outer electron e.g. Indium



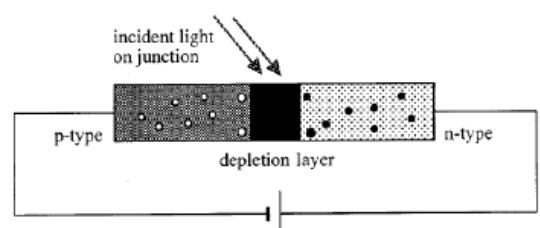An LED is a forward biased p-n junction. When an electron and a hole recombine. The electron moves from the conduction band into the valence band and emits a photon of light.



Reverse bias